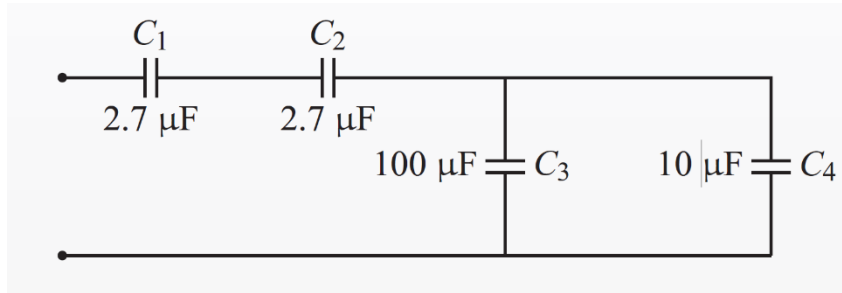


PHYS0525 Analog and Digital Electronics – Spring 2026

Assignment 2

Due Monday, Feb 2, 2026

1) Find the equivalent capacitance of the circuit drawn below.




$$\frac{1}{C_{12eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \frac{1}{C_{12eq}} = \frac{1}{2.7} + \frac{1}{2.7}$$

$$C_{12eq} = \left(\frac{2}{2.7}\right)^{-1} \Rightarrow 1.35 \mu F$$

$$C_{34eq} = C_3 + C_4 = 110 \mu F$$

$$\frac{1}{C_{eq}} = \frac{1}{C_{12}} + \frac{1}{C_{34}} = \left(\frac{1}{1.35 \mu F} + \frac{1}{110 \mu F}\right)^{-1} = 1.33 \mu F$$

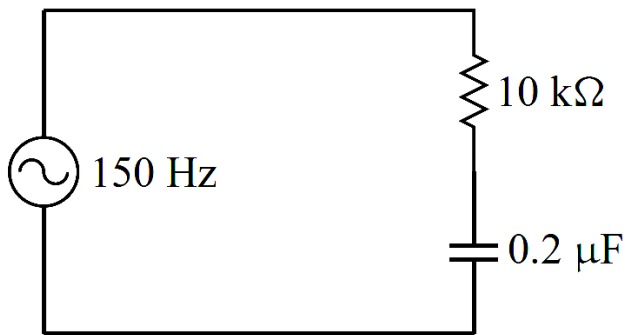2) Assuming the amplitude of the voltage source in the circuit below is 1 V, what is the amplitude of the voltage across the capacitor? What is the average power dissipated by the resistor (averaged over many cycles of the voltage source)?



$$V_C = V_a \cdot \frac{X_C}{Z}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi (150 \text{ Hz}) \cdot 0.2 \mu F} \Rightarrow 5305.16$$

$$Z = \sqrt{X_C^2 + R^2} = \sqrt{10 \text{ k}\Omega^2 + (5305.16)^2} \Rightarrow 113210$$

$$V_C = 1 \cdot \frac{5305.16}{113210.2} = 0.46816 \text{ V}$$

$$P_{avg} = (I_{rms})^2 \cdot R \quad I_{rms} = I_{peak} / \sqrt{2} \quad V_a / Z$$

$$= \frac{1}{113210} = 8.8331 \times 10^{-5} \text{ A} / \sqrt{2} = (6.24 \times 10^{-5} \text{ A})^2 \cdot [10^4] = 3.9 \times 10^{-6} \text{ W} = 3.9 \mu W$$

3) I have a circuit element with complex impedance $Z = R + \frac{1}{i\omega C}$, where $R = 100\Omega$, $C = 160 \text{ nF}$, and $\omega = 2\pi \times 10 \text{ kHz}$. Compute the real and imaginary parts of Z . Also compute the magnitude and phase of Z .

$$Z = R + \frac{1}{i\omega C}$$


(Real) (imaginary) $\rightarrow \frac{1}{i} = -i \Rightarrow \frac{1}{i\omega C} = -i\left(\frac{1}{\omega C}\right) = -i\left(\frac{1}{2\pi \times [10 \times 10^3 \text{ Hz}] \cdot 160 \cdot [10 \times 10^{-9} \text{ F}]}\right)$

$$\Rightarrow -i(99.471)$$

magnitude: $\sqrt{Re^2 + Im^2} \Rightarrow \sqrt{100^2 + 99.471^2} = 141.0477$

phase: $\arctan\left(\frac{Re}{-Im}\right) = \tan^{-1}\left(\frac{100 \Omega}{-99.471 \text{ A/V s}^{-1}}\right) = -1.576^\circ$

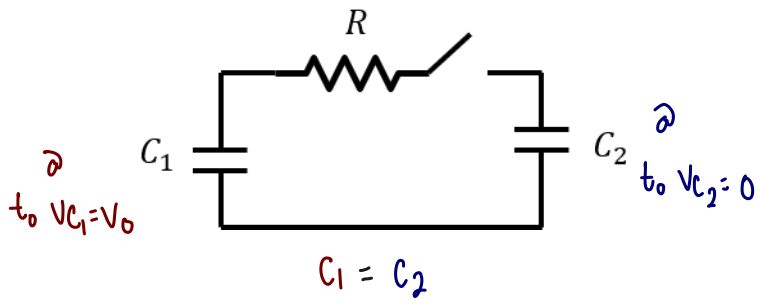4) In the circuit below, C_1 is initially charged to a voltage of $V_{C1}(t=0) = V_0$ and C_2 initially has no charge $V_{C2}(t=0) = 0$ and the switch is open. At time $t=0$ the switch is closed. Sketch $V_{C1}(t)$ and $V_{C2}(t)$ and compute the total amount of energy dissipated in the resistor. Assume the capacitance of the two capacitors is the same $C_1 = C_2 = C$.



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}, \quad C_1 = C_2: \frac{1}{C_{eq}} = \frac{2}{C}$$

$$\hookrightarrow C_{eq} = \frac{C}{2}$$

$$\text{at } t=\infty, V_{C1}(\infty) = V_{C2}(\infty)$$

$$Q_i = QC_0, \quad Q_f = QC_{1f} + QC_{2f}$$

$$CV_0 = 2CV_f, \quad V_f = \frac{CV_0}{2C} = \frac{V_0}{2}$$

$$V_0 - IR - V_C = 0$$

$$v(t) = VC_1(t) - VC_2(t) \Rightarrow v(t) = V(0)e^{-t/RC_{eq}} = V_0 e^{-2t/RC}$$

$$VC_1(t) = \frac{V_0}{2} + \frac{v(t)}{2} \Rightarrow \frac{V_0}{2} (1 + e^{-2t/RC})$$

$$VC_2(t) = \frac{V_0}{2} - \frac{v(t)}{2} \Rightarrow \frac{V_0}{2} (1 - e^{-2t/RC})$$

