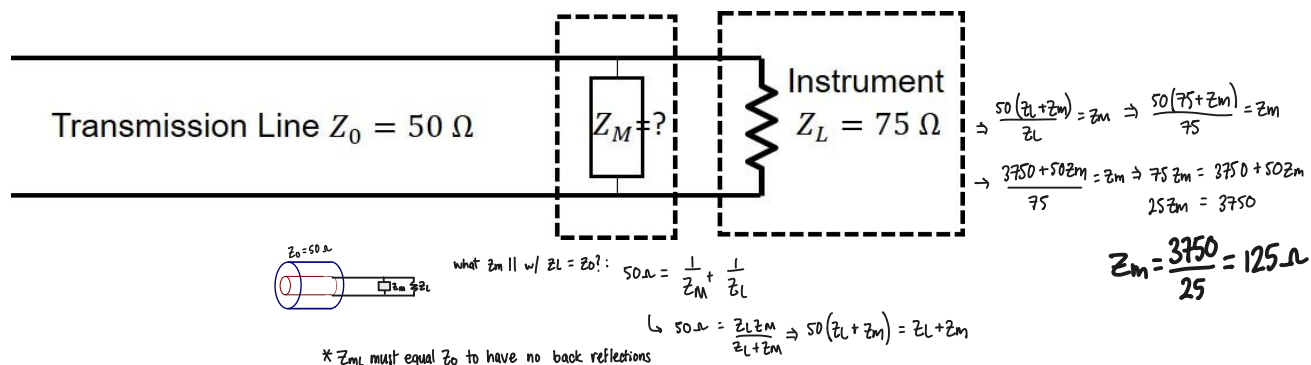


PHYS0525 Analog and Digital Electronics – Spring 2026

Assignment 4


Monday, Feb 16, 2026

1) Suppose you have a length of 50Ω cable and want to connect it to an instrument with a 75Ω input impedance. What circuit element (labeled Z_m in the figure below) could you add just prior to the instrument to impedance match this connection (i.e. have no back reflections into your 50Ω cable).



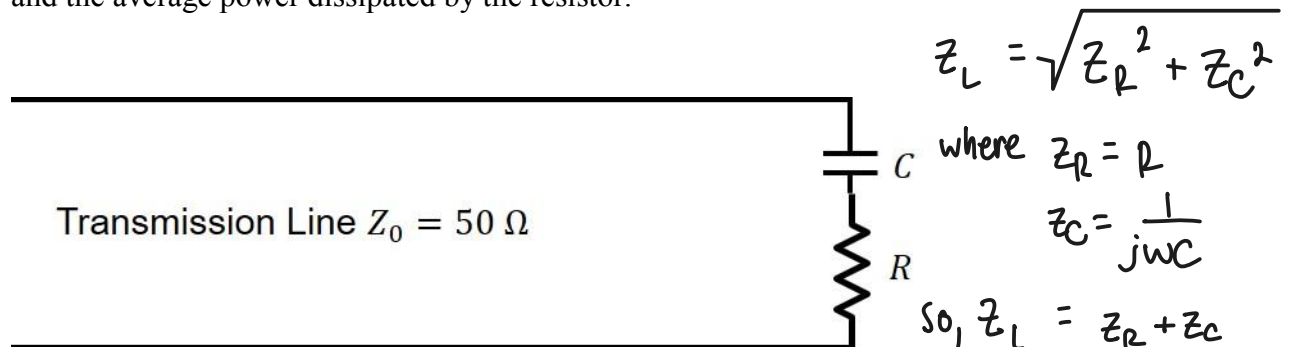2) A wave of frequency $\omega = 2\pi \times 1 \text{ MHz}$ and amplitude $V_0 = 1 \text{ V}$ is traveling down a 50Ω cable. The cable is terminated with a capacitor with a series combination of a capacitor $C = 10 \mu\text{F}$ and a resistor $R = 25 \Omega$.

- What is the amplitude and phase of the voltage of the reflected wave?
- What is the amplitude and phase of the current of the reflected wave?
- What is the amplitude of voltage across the resistor?
- Compute the average power in the incident wave, the average power in the reflected wave, and the average power dissipated by the resistor.



* can ignore C!
(insignificant contribution)

a.) $\frac{\hat{V}_R}{\hat{V}_0} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{-25}{75} = -\frac{1}{3} \approx \Gamma$

so amplitude $\approx \frac{1}{3}$, and phase $\approx 180^\circ$

b.) $\frac{\hat{I}}{\hat{I}_0} = \frac{V_0}{Z_0} = \frac{1}{50}$ w/ $\frac{1}{50} \cdot \frac{1}{| \Gamma |} = \hat{I} = \frac{1}{50} \cdot \frac{1}{3} = \frac{1}{150} \approx 0.667 \text{ A}$

and phase $\approx 0^\circ$

$$c.) \left. \begin{aligned} V_R &= I_L R \\ &= \frac{V_L}{Z_L} \cdot R \end{aligned} \right\} = V_L = V_0(1+\Gamma)$$

$$\text{so, } V_R = \frac{V_0(1+\Gamma)}{Z_L} \cdot R = \frac{1-\frac{1}{3}}{25} = \frac{2/3}{25} = 0.02666 \text{ A}$$

$$d.) P_{in} = \frac{V_0^2}{2 Z_0} = \frac{1}{100} \text{ W} \quad P_{ref.} = \Gamma^2 P_{in} = \frac{1}{9} \cdot 10 \text{ mW} = \frac{10}{9} \text{ mW}, \quad P_{res.} = \frac{1}{2} I_L^2 \cdot R^2$$

$$= 10 \text{ mW} \qquad \qquad \qquad = \frac{0.02666^2 \cdot 25}{2}$$

$$= 0.00889 \text{ W}$$


$$= 8.89 \text{ mW}$$

PHYS0525 Analog and Digital Electronics – Spring 2026

Assignment 4

Monday, Feb 16, 2026

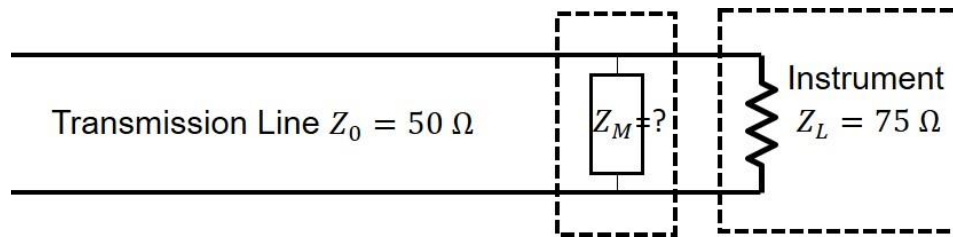1) Suppose you have a length of $50\ \Omega$ cable and want to connect it to an instrument with a $75\ \Omega$ input impedance. What circuit element (labeled Z_m in the figure below) could you add just prior to the instrument to impedance match this connection (i.e. have no back reflections into your $50\ \Omega$ cable).



2) A wave of frequency $\omega = 2\pi \times 1\ \text{MHz}$ and amplitude $V_0 = 1\ \text{V}$ is traveling down a $50\ \Omega$ cable. The cable is terminated with a capacitor with a series combination of a capacitor $C = 10\ \mu\text{F}$ and a resistor $R = 25\ \Omega$.

- What is the amplitude and phase of the voltage of the reflected wave?
- What is the amplitude and phase of the current of the reflected wave?
- What is the amplitude of voltage across the resistor?
- Compute the average power in the incident wave, the average power in the reflected wave, and the average power dissipated by the resistor.

