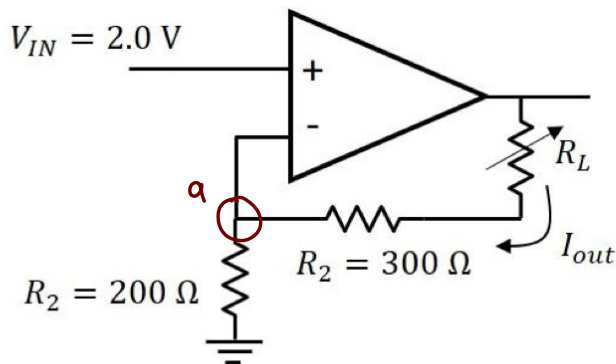


Assignment 8


Due Monday, April 6, 2026

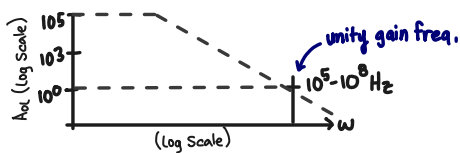- 1) The circuit below can be thought of as a voltage controlled current source.
 - (a) Show that the current, I_{out} , through the load resistor, R_L , is independent of the value of R_L .
 - (b) For $V_{in} = 2$ Volts, what is the value of I_{out} ?
 - (c) If the op amp has supply voltages $V_s = 10$ V and $-V_s = -10$ V, what is the maximum current that can be supplied to a 100Ω load resistor? What input voltage does this correspond to?



a.) Properties of op-amps

- Inputs are very high impedance ($10^6 - 10^{14} \Omega$)
(typically assume $Z_{in} \approx \infty$ [$1 - 100 \Omega$])
- Output impedance is low ($1 - 100 \Omega$)
(assume Z_{out} is negligible)
- output $-V_s < V_{out} < +V_s$
(typically assume A_{OL} is large $\rightarrow \infty$)



$$V_{th} > 0 \quad (V_{out} = +2V)$$

$$V_{th} < 0 \quad (V_{out} = -2V)$$

$$V^- = V^+ = V_{in}$$

• no current to inputs

∴ a: $\frac{V_{in} - 0}{200 \Omega} + \frac{V_{in} - V_L}{300 \Omega} = 0$

$$\hookrightarrow \frac{3V_{in}}{2} + (V_{in} - V_L) = 2V_{in} + 2V_{in} - 2V_L = 0$$

$$\hookrightarrow V_L = \frac{5}{2} V_{in}$$

$$\text{and } I_{out} = I \text{ @ } R_L = \frac{V_L - V_{in}}{300 \Omega} \Rightarrow \frac{\frac{5}{2} V_{in} - V_{in}}{300}$$

$$\text{so, } I_{out} = \frac{\frac{3}{2} V_{in}}{300} \Rightarrow \frac{V_{in}}{200} \quad (\text{independent of } L)$$

b.) For $V_{in} = 2V$: $I_{out} = \frac{2}{200} = \frac{1}{100} A = 0.01 A = 10 \text{ mA}$


c.) $V_{out} = V_L + I_{out} \cdot R_L$

$$\hookrightarrow V_{out} = \frac{5}{2} V_{in} + \frac{V_{in}}{200} \cdot 100$$

$$V_{out} = \frac{5}{2} V_{in} + \frac{1}{2} V_{in} = 3V_{in}$$

and $V_{in} = \pm 10V$, so $V_{out} \approx \frac{10}{3} V = 3.33V$

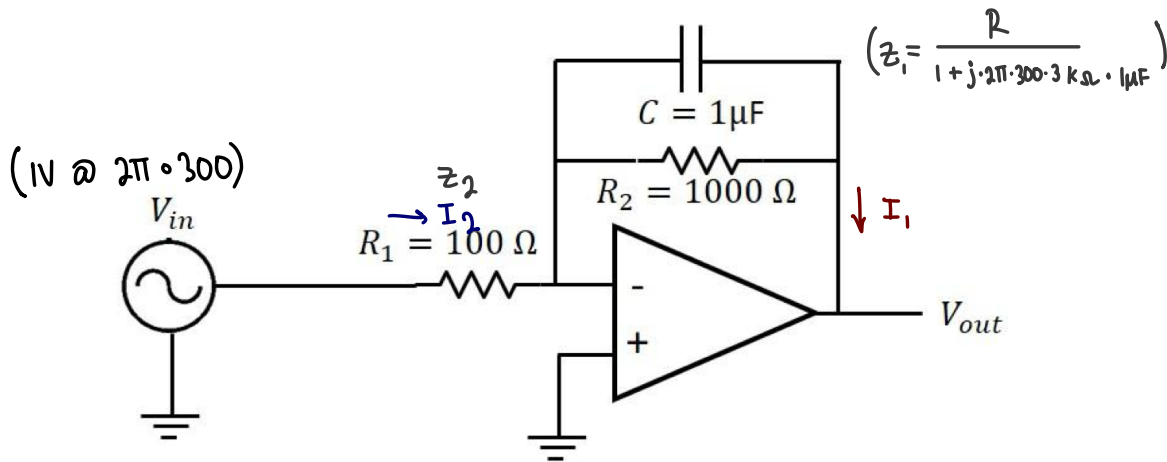2) The circuit below has an AC input voltage with an amplitude of 1V at a frequency $\omega = 2\pi \times 300 \text{ s}^{-1}$. What is the amplitude of the output voltage? You may assume the op-amp is ideal. (Hint: You can consider this circuit as an inverting amplifier with the gain given by the ratio of the feedback impedance to the input impedance.)



Golden Rule

$$V_{in}^+ = V_{in}^- = 0 \quad I_1 = I_2$$

$$I_2 = \frac{V_{in} - V_{in}^-}{R_2} = \frac{V_{in}}{R_2} = I_1$$

$$V_{out} = -I_1 R_1 = -\frac{V_{in}}{R_2} \cdot R_1$$

$$V_{out} = \left(-\frac{R_1}{R_2} \right) \cdot V_{in} \quad \text{Gain} \quad \approx \frac{|z_1|}{|z_2|} \cdot V_{in} \Rightarrow$$

Inverting Amplifier

$$\frac{\left| \frac{1}{1 + (j \frac{2\pi}{300} 1000 \cdot 1\text{E-}6\text{F})} \right|}{|100 \Omega|} \cdot 1\text{V} \Rightarrow \frac{1}{\sqrt{1 + (\frac{2\pi}{300} \cdot 1000 \cdot 1\text{E-}6)^2}} = 4.686 \cdot 1\text{V} \approx \underline{4.7\text{V}}$$