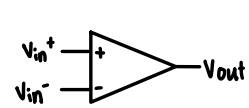


Op-amp devices and Digital Logic





$$V_{out} = A_{OL}(V_{in+} - V_{in-})$$

$$A_{OL} \gg 1$$



Golden Rule

$$V_{in+} = V_{in-} = 0 \quad I_1 = I_2$$


Input draws no current

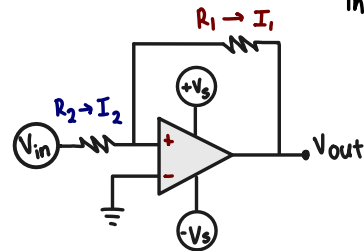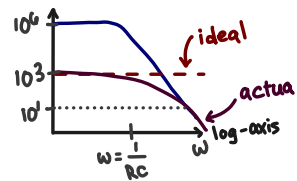


Comparator

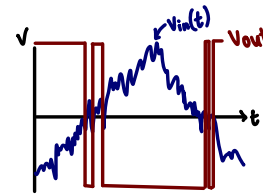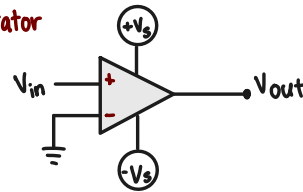

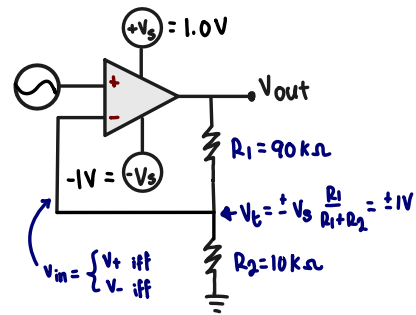Schmitt Trigger - Reduces Switching Behavior




Relaxing Oscillator


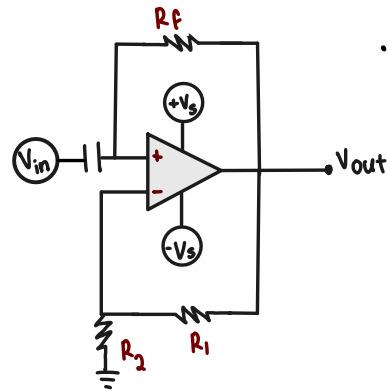


Assuming Starting Point

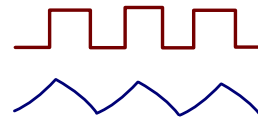- $V_{out} = +V_s$ + C uncharged
- $V_{in-} = 0 < V_{in+} = V_t = \frac{R_2}{R_1 + R_2} \cdot V_s$
- Since $V_{out} = V_s$ a current will flow through R_f + start to charge C with $\tau = R_f C$
- eventually $V_{in-} > V_{in+} = V_t$
- then $V_{out} \rightarrow -V_s$
- Cap starts to discharge
- then output flips back



555 Timer Integrated Circuit

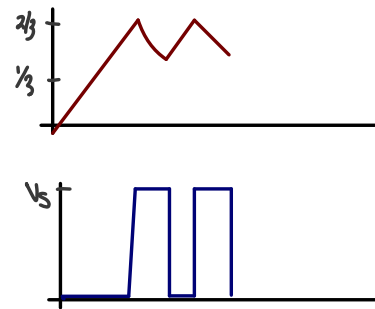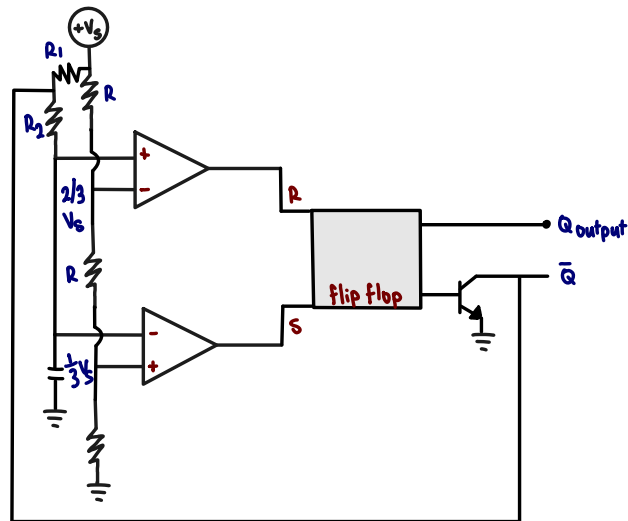

Digital Logic

a 'bit' of information - 0 or 1 state




NAND




Input		Output
A	B	
0	0	1
0	1	1
1	0	1
1	1	0

NOR

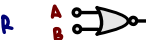

Input		Output
A	B	
0	0	1
0	1	0
1	0	0
1	1	0

Bistable Memory
'Flip-Flop'

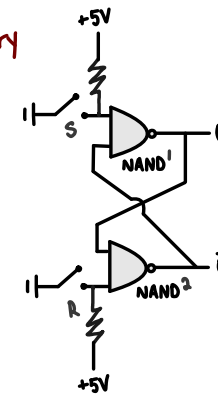

With both switches open

Guess: what if $Q = 0$
then $\bar{Q} = 1$

then both inputs are high V

Guess: what if $Q = 1$
then $\bar{Q} = 0$

then inputs of 1 are 0 or 1 V

Input		Output	
S	R	Q	$\bar{Q}$
0	0	1	0
0	1	0	1
1	0	1	0
1	1	0	1

Logic Gate

TRUTH TABLE

NOT



Input	Output
A	
0	1
1	0

AND




Input		Output
A	B	
0	0	0
0	1	0
1	0	0
1	1	1

OR



Input		Output
A	B	
0	0	0
0	1	1
1	0	1
1	1	1

XOR

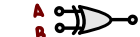

Input		Output
A	B	
0	0	0
0	1	1
1	0	1
1	1	0

→ now close S
then $Q = 1 + \bar{Q} = 0$

→ now open S
nothing changes!

→ now close R
then $Q = 1 + \bar{Q} = 0$

→ now open R
nothing changes

Input		Output
A	B	
0	0	1
0	1	1
1	0	1
1	1	0